 


# Sequential Logic Design

- Design the following circuits using Verilog and create a testbench for each design to check its functionality. **Create a do file for question 5 only.**

- Testbenches are advised to be a mix between randomization and directed testing taken into consideration realistic operation for the inputs. Apply self-checking condition in the testbench for at least one of the design below.

- 1) Implement D-Type Flip-Flop with active high Enable.




Input	Output
D, E, CLK	Q

## Truth Table

E	CLK	D	$Q_{n+1}$
0	X	X	$Q_n$
1	not Rising	X	$Q_n$
1	↑	D	D

 - 2) Implement Data Latch with active low Clear



Input	Output
CLR, D, G	Q

### Truth Table

CLR	G	D	Q
0	X	X	0
1	0	X	Q
1	1	D	D

3) Implement the following latch as specified below

### Parameters

LAT\_WIDTH: Determine the width of input data and output q

### Ports

Name	Type	Description
aset	Input	Asynchronous set input. Sets q[] output to 1.
data[]		Data Input to the D-type latch with width LAT_WIDTH
gate		Latch enable input
aclr		Asynchronous clear input. Sets q[] output to 0.
q[]	Output	Data output from the latch with with LAT_WIDTH

If both aset and aclr are both asserted, aclr is dominant.

4)

A. Implement T-type (toggle) Flipflop with active low asynchronous reset. T-Flipflop has input t, when t input is high the outputs toggle else the output values do not change.

- Inputs: t, rstn, clk
- Outputs: q, qbar


B. Implement Asynchronous D Flip-Flop with Active low reset

- Inputs: d, rstn, clk
- Outputs: q, qbar


C. Implement a parameterized asynchronous FlipFlop with Active low reset with the following specifications.

- Inputs: d, rstn, clk
- Outputs: q, qbar
- Parameter: FF\_TYPE that can take two valid values, DFF or TFF. Default value = "DFF". Design should act as DFF if FF\_TYPE = "DFF" and act as TFF if FF\_TYPE = "TFF". When FF\_TYPE equals "DFF", d input acts as the data input "d", and when FF\_TYPE equals "TFF", d input acts the toggle input "t".

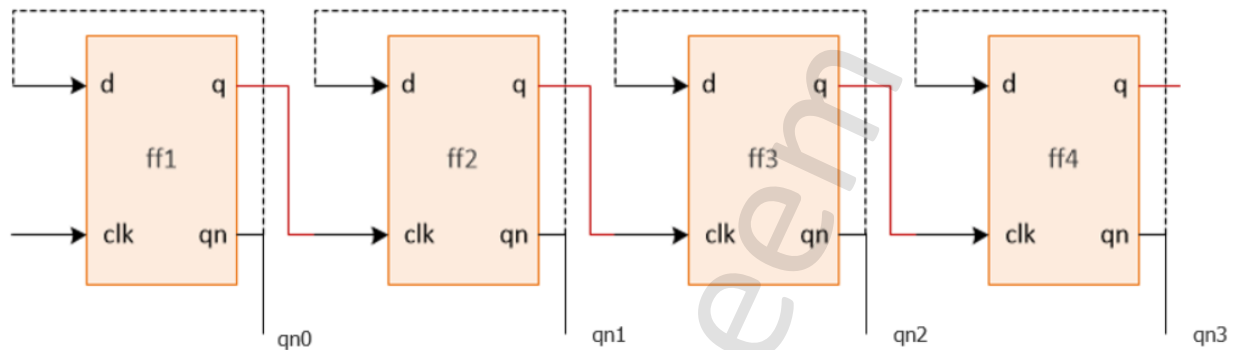- D. Test the above parameterized Design using 2 testbenches, testbench 1 that overrides the design with FF\_TYPE = "DFF" and the testbench 2 overrides parameter with FF\_TYPE = "TFF"
- Testbench 1 should instantiate the design of part B. as a golden model to check for the output of the parameterized design with FF\_TYPE = "DFF"
  - Testbench 2 should instantiate the design of part A. as a golden model to check for the output of the parameterized design with FF\_TYPE = "TFF"
- 5) Implement the 4-bit Ripple counter shown below using structural modelling (Instantiate the Dff from question 4 part B where the output is taken from the qn as shown below)
- Inputs: clk, rstn;
  - Outputs: [3:0] out;



 - 6) Implement the following SLE (sequential logic element)



Input		Output
Name	Function	Q
D	Data	
CLK	Clock	
EN	Enable	
ALn	Asynchronous Load (Active Low)	
ADn*	Asynchronous Data (Active Low)	
SLn	Synchronous Load (Active Low)	
SD*	Synchronous Data	
LAT*	Latch Enable	

**\*Note:** ADn, SD and LAT are static signals defined at design time and need to be tied to 0 or 1.

### **Truth Table**

ALn	ADn	LAT	CLK	EN	SLn	SD	D	Q <sub>n+1</sub>
0	ADn	X	X	X	X	X	X	!ADn
1	X	0	Not rising	X	X	X	X	Qn
1	X	0	↑	0	X	X	X	Qn
1	X	0	↑	1	0	SD	X	SD
1	X	0	↑	1	1	X	D	D
1	X	1	0	X	X	X	X	Qn
1	X	1	1	0	X	X	X	Qn
1	X	1	1	1	0	SD	X	SD
1	X	1	1	1	1	X	D	D

### Deliverables:

- 1) The assignment should be submitted as a PDF file with this format  
<your\_name>\_Assignment3 for example Kareem\_Waseem\_Assignment3
- 2) Snippets from the waveforms captured from QuestaSim for each design with inputs assigned values and output values visible.

Note that your document should be organized as 6 sections corresponding to each design above, and in each section, I am expecting the Verilog code, and the waveforms snippets