

# Assignment 3

(Under supervision of Eng: Karim Wassem)

Q1]

```
question1.v X question1_tb.v
Assignment_3 > q1 > question1.v
1 module q1(E,D,CLK,Q);
2
3 input E,D,CLK; // E is an enable signal
4 output reg Q;
5
6 always @(posedge CLK) begin
7
8     if(E)
9         Q<=D;
10
11 end
12
13 endmodule
14
15
```

```
|VSIM 46> run -all
# AT time= 0 D=0 enable=0 Q=x
# AT time= 50 D=0 enable=1 Q=x
# AT time= 75 D=0 enable=1 Q=0
# AT time= 100 D=1 enable=1 Q=0
# AT time= 125 D=1 enable=1 Q=1
# AT time= 200 D=1 enable=0 Q=1
# AT time= 250 D=1 enable=1 Q=1
# AT time= 300 D=0 enable=1 Q=1
# AT time= 325 D=0 enable=1 Q=0
# AT time= 350 D=1 enable=0 Q=0
# ** Note: $stop : D:/VS_code/Verilog codes/Assignment_3/q1/question1_tb.v(29)
# Time: 500 ns Iteration: 1 Instance: /q1_tb
```

Figure (1) : Verilog code

Figure (2) : transcript

 


Figure (3): waveform

```

question1.v  question1_tb.v X
Assignment_3 > q1 > question1_tb.v
1  module q1_tb();
2
3  reg d,en,clk;
4  wire q;
5  integer i;
6
7  q1 DUT (.D(d),.E(en),.CLK(clk),.Q(q));
8
9  initial begin
10 clk=0;
11 forever
12 #25 clk=~clk;    // this mean that time period of clock=50 ns
13
14 end
15
16 initial begin
17
18 d=0;
19 en=0;
20
21 for(i=0;i<10;i=i+1) begin
22
23 @(negedge clk);
24 d=$random;
25 en=$random;
26
27 end
28
29 $stop;
30
31 end
32
33 initial
34 $monitor("AT time= %g\t D=%b \t enable=%b \tQ=%b",$time,d,en,q);
35
36 endmodule

```

Figure(4) : testbench

➔ As we see from these figures that we use randomized values for the input to produce the output of the D flip flop with monitoring it's values as shown in figure (2) "transcript".

## Q2]

```
≡ question2.v X ≡ question2_tb.v
Assignment_3 > q2 > ≡ question2.v
1  module q2(clear,G,D,Q);
2
3  input clear,G,D; // G is an enable signal
4  output reg Q;
5
6  always @(clear or G or D) begin
7
8      if(~clear)
9          Q<=0;
10     else if(G)
11         Q<=D;
12
13 end
14
15 endmodule
```

Figure(5): Verilog code

```
≡ question2.v ≡ question2_tb.v X
Assignment_3 > q2 > ≡ question2_tb.v
1  module q2_tb();
2
3  reg CLR,D,G;
4  wire q;
5  integer i;
6
7  q2 DUT (.D(D),.clear(CLR),.G(G),.Q(q));
8
9  initial begin
10
11     for(i=0;i<10;i=i+1) begin
12         D=$random;
13         CLR=$random;
14         G=$random;
15         #50;
16     end
17
18     $stop;
19
20 end
21
22 initial
23 $monitor("AT time= %g\t D=%b \tclear=%b\tenable(G)=%b\tQ=%b", $time,D,CLR,G,q);
24
25 endmodule
```

Figure (6): testbench code

➔ This design represent a D latch with active enable(G) signal and active low (clear) where as shown in figure (6) we test the design using randomized values of inputs.

 


Figure (7): waveform

Q3]

 


Figure (8): waveform

```

question3.v X question3_tb.v
Assignment_3 > q3 > question3.v
1  module q3(data,gate,aclr,aset,q);
2
3  parameter LAT_WIDTH=1;
4  input [LAT_WIDTH-1:0]data;
5  input gate,aclr,aset;
6  output reg [LAT_WIDTH-1:0] q;
7
8  always @(*) begin
9
10 if(aclr)
11 q<=0;
12 else begin
13 if(aset)
14 q<=1;
15 else if(gate)
16 q<=data;
17
18 end
19
20 end
21
22 endmodule

```

Figure (9): Verilog code

```

question3.v X question3_tb.v X
Assignment_3 > q3 > question3_tb.v
1  module q3_tb();
2
3  reg DATA,ACLR,ASET,GATE;
4  wire Q;
5  integer i;
6
7  q3 DUT (.data(DATA),.gate(GATE),.aclr(ACLR),.aset(ASET),.q(Q));
8
9  initial begin
10
11 for(i=0;i<10;i=i+1) begin
12 DATA=$random;
13 ACLR=$random;
14 ASET=$random;
15 GATE=$random;
16 #50;
17 end
18
19 $stop;
20
21 end
22
23 initial
24 $monitor(" Data=%b \tclear=%b\tset=%b\tgate(enable)=%b\tQ=%b",DATA,ACLR,ASET,GATE,Q);
25
26 endmodule

```

Figure (10) : testbench code

➔ Figure (8&9&10) shows the waveform and codes for question3 .Also as shown in figure (10) we use the randomized values for inputs to detect the output of the D latch.

Q4]

```

≡ tff.v  ≡ dff.v  X  ≡ parameterized_ff.v
Assignment_3 > q4 > ≡ dff.v
1  module dff(d,clk,rst_n,q,qbar);
2
3  input d,clk,rst_n;
4  output reg q;
5  output qbar;
6
7  always @(posedge clk or negedge rst_n) begin
8
9  if(~rst_n)
10 q<=0;
11 else
12 q<=d;
13
14 end
15
16 assign qbar=~q;
17
18 endmodule

```

Figure (11): D flipflop code

```

≡ tff.v  X  ≡ dff.v  ≡ parameterized_ff.v
Assignment_3 > q4 > ≡ tff.v
1  module tff(t,clk,rst_n,q,qbar);
2
3  input t,clk,rst_n;
4  output reg q;
5  output qbar;
6
7  always @(posedge clk or negedge rst_n) begin
8
9  if(~rst_n)
10 q<=0;
11 else if(t)
12 q<=~q;
13
14 end
15
16 assign qbar=~q;
17
18 endmodule

```

Figure (12): T flipflop code

```

≡ tff.v  ≡ dff.v  ≡ parameterized_ff.v X  ≡ test1_tb.v  ≡ test2_tb.v
Assignment_3 > q4 > ≡ parameterized_ff.v
1  module para_ff(d,clk,rst_n,q,qbar);
2
3  parameter FF_TYPE="DFF";
4  input d,clk,rst_n;
5  output q,qbar;
6
7  generate
8      case(FF_TYPE)
9
10 "DFF": dff f1(.d(d),.clk(clk),.rst_n(rst_n),.q(q),.qbar(qbar));
11
12 "TFF": tff f2(.t(d),.clk(clk),.rst_n(rst_n),.q(q),.qbar(qbar));
13
14 endcase
15
16 endgenerate
17
18
19 endmodule

```

Figure (13): parameterized flip flop code

```

tff.v  dff.v  parameterized_ff.v  test1_tb.v  test2_tb.v  Genera
Assignment_3 > q4 > test1_tb.v
1  module test1_tb();
2  parameter N1="DFF";
3  reg D,CLK,RST_N;
4  wire Q,QBAR;
5  wire q_expected,qbar_expected;
6  integer i;
7
8  para_ff #(.FF_TYPE(N1)) DUT1 (.d(D),.clk(CLK),.rst_n(RST_N),.q(Q),.qbar(QBAR));
9  dff DUT2 (.d(D),.clk(CLK),.rst_n(RST_N),.q(q_expected),.qbar(qbar_expected));
10
11 initial begin
12 CLK=0;
13 forever
14 #25 CLK=~CLK;    // this mean that the period of the clock =50ns
15 end
16
17 initial begin
18 RST_N=0;
19 D=0;
20 #50;
21 RST_N=1;
22 for(i=0;i<10;i=i+1) begin
23 @(negedge CLK);
24 D=$random;
25 if(Q!=q_expected||QBAR!=qbar_expected) begin
26 $display("Error,this design is incorrect!!");
27 $stop;
28 end
29 end
30 $stop;
31 end
32
33 initial
34 $monitor("D=%b\treset=%b\tQ=%b\tQ_expected=%b\tQbar=%b\tQbar_expected=%b",D,RST_N,Q,q_expected,QBAR,qbar_expected);
35
36 endmodule
37

```

Figure (14): first testbench for the first design (DFF)

 


Figure (15) : waveform for the first testbench

```

VSIM 96> run -all
# D=0   reset=0 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# D=0   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# D=1   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# D=1   reset=1 Q=1      Q_expected=1 Qbar=0 Qbar_expected=0
# D=0   reset=1 Q=1      Q_expected=1 Qbar=0 Qbar_expected=0
# D=0   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# D=1   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# D=1   reset=1 Q=1      Q_expected=1 Qbar=0 Qbar_expected=0
# ** Note: $stop      : D:/VS_code/Verilog codes/Assignment_3/q4/test1_tb.v(40)
#   Time: 500 ns   Iteration: 1   Instance: /test1_tb
# Break in Module test1_tb at D:/VS_code/Verilog codes/Assignment_3/q4/test1_tb.v line 40

```

Figure (16): transcript for the first design using DFF

```

Assignment_3 > q4 > test2_tb.v
1  module test2_tb();
2  parameter N2="TFF";
3  reg D,CLK,RST_N;
4  wire Q,QBAR;
5  wire q_expected,qbar_expected;
6  integer i;
7
8  para_ff #(.FF_TYPE(N2)) DUT3 (.d(D),.clk(CLK),.rst_n(RST_N),.q(Q),.qbar(QBAR));
9  tff DUT4 (.t(D),.clk(CLK),.rst_n(RST_N),.q(q_expected),.qbar(qbar_expected));
10
11 initial begin
12   CLK=0;
13   forever
14     #25 CLK=~CLK;
15 end
16
17 initial begin
18   RST_N=0;
19   D=0;
20   #50;
21   RST_N=1;
22   for(i=0;i<10;i=i+1) begin
23     @(negedge CLK);
24     D=$random;
25     if(Q!=q_expected||QBAR!=qbar_expected) begin
26       $display("Error,this design is incorrect!!");
27       $stop;
28     end
29   end
30   $stop;
31 end
32
33 initial
34   $monitor("T=%b\treset=%b\tQ=%b\tQ_expected=%b\tQbar=%b\tQbar_expected=%b",D,RST_N,Q,q_expected,QBAR,qbar_expected);
35
36 endmodule

```

Figure (17) : second testbench for the second design (TFF)



 


Figure (18) : waveform for the second design

```

VSIM 102> run -all
# T=0   reset=0 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# T=0   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# T=1   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# T=1   reset=1 Q=1      Q_expected=1 Qbar=0 Qbar_expected=0
# T=1   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# T=1   reset=1 Q=1      Q_expected=1 Qbar=0 Qbar_expected=0
# T=1   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# T=1   reset=1 Q=1      Q_expected=1 Qbar=0 Qbar_expected=0
# T=1   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# T=0   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# T=1   reset=1 Q=0      Q_expected=0 Qbar=1 Qbar_expected=1
# T=1   reset=1 Q=1      Q_expected=1 Qbar=0 Qbar_expected=0
# ** Note: $stop      : D:/VS_code/Verilog codes/Assignment_3/q4/test2_tb.v(40)
#   Time: 500 ns   Iteration: 1   Instance: /test2_tb
# Break in Module test2_tb at D:/VS_code/Verilog codes/Assignment_3/q4/test2_tb.v line 40

```

Figure (19): transcript for the second design

- ➔ As shown in the figures (14 & 17) “two testbenches” we use the randomization method but with self checking as we test our designs using two golden references (DFF & TFF).
- ➔ Moreover, the figures(16 & 19) “two transcript” verify that our designs operate well due to the equality between the out\_dut(Q) and the expected output from the golden reference design (Q\_expected).

## Q5]

```

≡ dff.v  ≡ question5.v X  ≡ question5_tb.v
Assignment_3 > q5 > ≡ question5.v
1  module counter (RST_N,CLK,out);
2
3  input RST_N,CLK;
4  output [3:0] out;
5  wire w1,w2,w3;
6
7  dff f1(.d(out[0]),.clk(CLK),.rst_n(RST_N),.q(w1),.qbar(out[0]));
8
9  dff f2(.d(out[1]),.clk(w1),.rst_n(RST_N),.q(w2),.qbar(out[1]));
10
11 dff f3(.d(out[2]),.clk(w2),.rst_n(RST_N),.q(w3),.qbar(out[2]));
12
13 dff f4(.d(out[3]),.clk(w3),.rst_n(RST_N),.q(),.qbar(out[3]));
14
15
16 endmodule
17

```

Figure (20): design code

```

≡ dff.v  ≡ question5.v  ≡ question5_tb.v X
Assignment_3 > q5 > ≡ question5_tb.v
1  module counter_tb();
2
3  reg reset,clk;
4  wire [3:0] out_dut;
5
6  counter DUT(.RST_N(reset),.CLK(clk),.out(out_dut));
7
8  initial begin
9  clk=0;
10 forever
11 #25 clk=~clk;
12 end
13
14 initial begin
15 reset=0;
16 #50;          // #50 mean one clock cycle (to reset the counter)
17 reset=1;
18 #1000;        // #1000 mean 20 clock cycles
19 $stop;
20 end
21
22 initial
23 $monitor(" reset=%b \t out_dut=%b ",reset,out_dut);
24
25 endmodule

```

Figure (21) : testbench code

```

≡ dff.v  ≡ question5.v  ≡ question5_tb.v  ≡ main.do X
Assignment_3 > q5 > ≡ main.do
1  vlib work
2  vlog question5.v question5_tb.v
3  vsim -voptargs=+acc work.counter_tb
4  add wave *
5  run -all

```

Figure (22) : do file

```

----- /main.do -----
Questasim> do main.do
# ** Warning: (vlib-34) Library already exists at "work".
# Errors: 0, Warnings: 1
# Questasim-64 vlog 2021.1 Compiler 2021.01 Jan 19 2021
# Start time: 05:45:34 on Jul 20,2023
# vlog -reportprogress 300 question5_tb.v
# -- Compiling module counter
# -- Compiling module counter_tb
#
# Top level modules:
#   counter_tb
# End time: 05:45:34 on Jul 20,2023, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
# vsim -voptargs="+acc" work.counter_tb
# Start time: 05:45:36 on Jul 20,2023
# ** Note: (vsim-3813) Design is being optimized due to module recompilation...
# Loading work.counter_tb(fast)
# Loading work.counter(fast)
# Loading work.dff(fast)
# Loading work.dff(fast__l)
# reset=0    out_dut=1111
# reset=1    out_dut=1111
# reset=1    out_dut=0000
# reset=1    out_dut=0001
# reset=1    out_dut=0010
# reset=1    out_dut=0011
# reset=1    out_dut=0100
# reset=1    out_dut=0101
# reset=1    out_dut=0110
# reset=1    out_dut=0111
# reset=1    out_dut=1000
# reset=1    out_dut=1001
# reset=1    out_dut=1010
# reset=1    out_dut=1011
# reset=1    out_dut=1100
# reset=1    out_dut=1101
# reset=1    out_dut=1110
# reset=1    out_dut=1111
# reset=1    out_dut=0000
# reset=1    out_dut=0001
# reset=1    out_dut=0010
# reset=1    out_dut=0011
# ** Note: $stop      : question5_tb.v(19)
#   Time: 1050 ns  Iteration: 0  Instance: /counter_tb
# Break in Module counter_tb at question5_tb.v line 19

```

Figure (23): transcript using do command

 


Figure (24): waveform

## Q6]

```

question6.v X question6_tb.v
Assignment_3 > q6 > question6.v
1  module SLE(ALn,ADn,LAT,CLK,EN,SLn,SD,D,Q);
2
3  input  ALn,ADn,LAT,CLK,EN,SLn,SD,D;
4  output reg Q;
5
6  always @(posedge CLK or negedge ALn) begin
7
8  if(~ALn)
9  |   Q<=~ADn;
10
11 else if(!LAT)
12 case({EN,SLn})
13 2'b10:Q<=SD;
14 2'b11:Q<=D;
15 endcase
16
17 end
18
19 always @(*) begin
20
21 if(LAT) begin
22 |   if(~ALn)
23 |   |   Q<=~ADn;
24 else begin
25 case({CLK,EN,SLn})
26 3'b110:Q<=SD;
27 3'b111:Q<=D;
28 endcase
29
30 end
31
32 end
33
34 end
35
36 endmodule

```

Figure (25): design verilog code

```

question6.v X question6_tb.v
Assignment_3 > q6 > question6_tb.v
1  module SLE_tb();
2
3  reg d,clk,en,aln,adn,sln,sd,lat;
4  wire q;
5  integer i;
6
7  SLE DUT(.D(d),.CLK(clk),.EN(en),.ALn(aln),.ADn(adn),.SLn(sln),.SD(sd),.LAT(lat),.Q(q));
8
9  initial begin
10 clk=0;
11 forever
12 #25 clk=~clk;
13 end
14
15 initial begin
16
17     aln=0; adn=0; d=0; en=0; sln=0; sd=0; lat=0;
18     #40;
19     aln=1;
20     for(i=0;i<10;i=i+1) begin
21
22         d=$random;
23         adn=$random;
24         en=$random;
25         sln=$random;
26         sd=$random;
27         lat=$random;
28         #50;
29     end
30 $stop;
31 end
32
33 initial
34 $monitor(" D=%b\t enable=%b\t SLn=%b\t SD=%b \t lat=%b\t out_dut=%b",d,en,sln,sd,lat,q);
35
36 endmodule

```

Figure (26): testbench code

➔ The above figures show the design and the testbench where in this case we use randomized input without self checking

➔ In addition to that the wave form snippet for this design is shown below “figure (27)”

 


Figure (27) : waveform